

Electronic Measurements And Instrumentation (MID II :TASK)

Name: B. Praveen

Roll Number: 22R05A0505

Branch: CSE

TASK: Design Wheatstone Bridge Measurement

A Wheatstone bridge is a classic electrical circuit used to measure unknown electrical resistances by balancing two legs of a bridge circuit. Here's a step-by-step guide to designing a Wheatstone bridge measurement system:

Components Needed:

Four resistors (R_1 , R_2 , R_3 , R_x)

A voltage source (V)

A galvanometer or voltmeter

Step-by-Step Design:

1. Circuit Diagram:

Draw a diamond-shaped circuit with four resistors forming the sides.

Connect the voltage source across the top and bottom nodes of the diamond.

Connect the measuring device (galvanometer or voltmeter) across the middle nodes (between R_1 and R_2 , and R_3 and R_x).

2. Resistor Configuration:

Let R_1 and R_2 be known resistors.

Let R_3 be a variable resistor (or a known resistor for some configurations).

Let R_x be the unknown resistor you want to measure.

3. Balancing the Bridge:

Adjust R_3 until the galvanometer shows zero current (or the voltmeter shows zero voltage).

At this balanced condition, the ratio of the resistances in one leg is equal to the ratio in the other leg:

$$\frac{R_1}{R_2} = \frac{R_3}{R_x}$$

4. Calculate Unknown Resistance:

Once the bridge is balanced, use the relationship:

If R_1 , R_2 , and R_3 are known, R_x can be easily calculated.

$$R_x = R_3 \left(\frac{R_2}{R_1} \right)$$

- $R_1 = 1\text{ k}\Omega$
- $R_2 = 1\text{ k}\Omega$
- R_3 is a variable resistor
- $V = 10\text{ V}$

You adjust R_3 until the galvanometer reads zero. At this balanced condition, suppose R_3 is adjusted to $2\text{ k}\Omega$. Then, the unknown resistor R_x can be calculated as:

$$R_x = R_3 \left(\frac{R_2}{R_1} \right) = 2\text{ k}\Omega \left(\frac{1\text{ k}\Omega}{1\text{ k}\Omega} \right) = 2\text{ k}\Omega$$

Thus, $R_x = 2\text{ k}\Omega$.

